

# COL 215 : Hardware Assignment 3

Tejas Anand, Kashish Goel

November 2022

## 1 Introduction

- In this assignment our objective was to implement Matrix Multiplication on the Basys3 FPGA Board.
- This assignment involves the design and integration of memories, registers and multiplier-accumulator components (MAC) in our design.

## 2 Problem Statement

Given two input matrices of size 128x128 and 8-bit unsigned integer, design a core in VHDL which perform matrix multiplication given input matrices.

## 3 Initial Thoughts...

- Entire Matrix Multiplication can be divided into separate vector by vector multiplications.
- We will design a Matrix Accumulator block, which will be driven by a clock that will read from the registers, compute the product and accumulate it to the existing sum.
- We will make 2 registers that will read from the ROM
- The timings of reading, computing and writing will be controlled by making states and changing those states via clocks. This will be our FSM.
- Our FSM will have 5 states namely, *read*, *compute*, *write*, *countreset* and *reset*. These states will be explained later.

## 4 Designing Individual Components

### 4.1 Register

A register has a clock input, bus-width, input data, write enable and output signal. output signal stores the value of the input when clock has a *rising\_edge* and write enable is 1. We can read from the register when write enable is 0.

```
entity reg is
generic (bus_width : integer );
Port (clk : in std_logic;
      din : in std_logic_vector(bus_width-1 downto 0);
      we : in std_logic;
      dout : out std_logic_vector(bus_width-1 downto 0) );
end reg;
architecture Behavioral of reg is
begin
process(clk)
begin
if rising_edge(clk) and we = '1' then
    dout<=din;
end if;
```

```
end process;
```

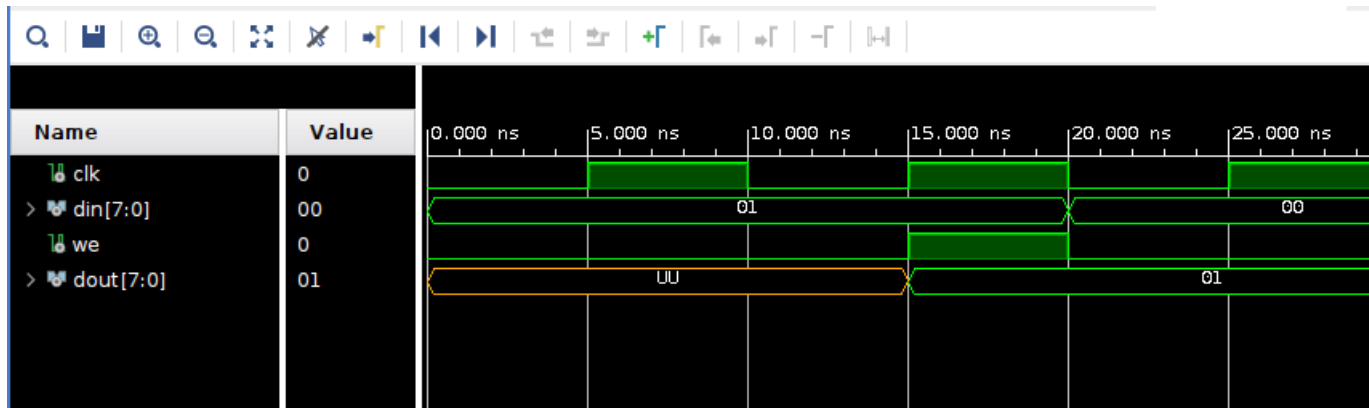


Figure 1: Register Test Simulation. We see that dout latches din when rising\_edge occurs and we = 1. After we = 0 , dout is not affected by din

## 4.2 Matrix Accumulate Block (MAC)

- MAC has a clock input, 2 numbers of type *std\_logic\_vector* as input, a control signal, an enable signal and a sum output.
- Control signal acts as a reset, when it is 1 we reset the sum to 0.
- We Accumulate the product of the numbers only when we have a rising edge of the clock and enable signal is 1.

```
process(clk,en,cntrl)
begin
if cntrl = '1' then
    sum_sig<="0000000000000000";
elsif rising_edge(clk) and en = '1' then
    sum_sig<= std_logic_vector(UNSIGNED(sum_sig)+UNSIGNED(num1)*UNSIGNED(num2));
end if;
end process;
sum<=sum_sig;
end Behavioral;
```

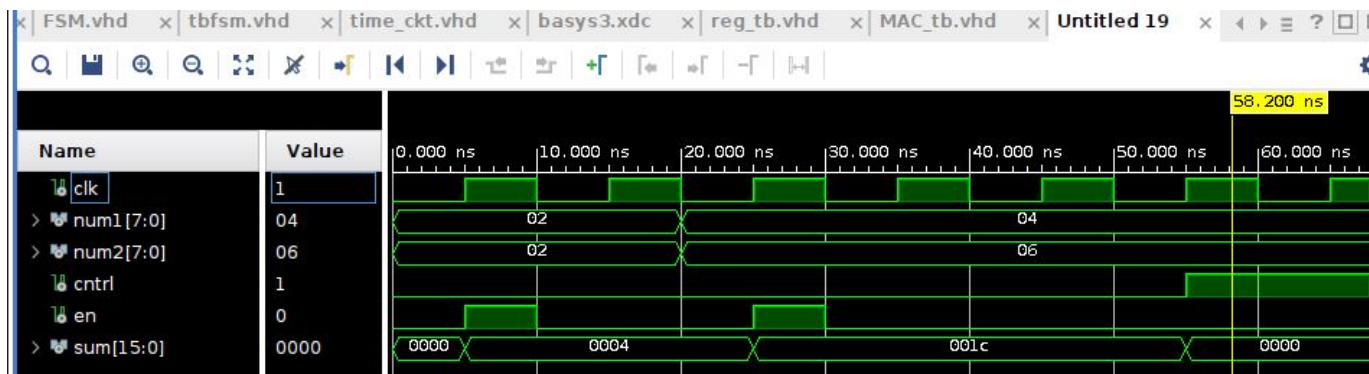


Figure 2: A Test Simulation for MAC

We can see 4 (2\*2) being accumulated at 5 ns , 24 (4\*6) is accumulated at 15 ns when en = 1 and sum being reset when cntrl = 1

### 4.3 Read Only Memory (ROM)

- We synthesized ROM using the IP catalog.
- ROM has a clock signal as input, an address input and a data output.
- For Our use case , address is at max  $128 * 128 = 16384$  which is equal to  $2^{14}$ . So we require 14 bits in our address . We are storing 8-bit numbers so output would be 8 bits at max.

 


Figure 3: A Test Simulation for ROM

We see at 5 ns, read is showing data at 5th index, When address changes to 1, read changes to data at 1st index.

### 4.4 Random Access Memory

- We synthesized RAM using the IP catalog.
- It has along with clk, address as input also write enable and din signals.
- When write enable is 0 it acts as ROM, when write enable is 1 it writes into the memory.

## 5 Putting everything together and Designing the Finite State Machine

- In the FSM , we will store the state of our computation using three integers  $i, j, k$
- Since the matrices are given in column major form, the index of  $a_{ij}$  is  $128j + i$
- For fixed  $(i, j)$  ,  $k$  is the index in the sum  $\sum a_{ik} b_{kj}$
- We start from the read state , when  $i = 0, k = 0$  and  $j = 0$ . We enable wreg which is the write register signal. Registers now have been written. In the next clock cycle we go to compute state for accumulation
- In compute state we increment  $k$  by 1 and set comp\_enable to 1. If  $k = 128$ , this means all terms have been accumulated. We then go to write state. If  $k < 127$ , we again go to read state to read the next term.
- In write state we enable wram, ram write signal to 1 and disable the computation. From the write state we always go to the countreset state
- In the countreset state we reset  $k$  to 0 and increment  $i$  if  $i < 127$  else we increment  $j$ . This basically means we are moving to the next pair of indices in the column major form of the resultant matrix.
- If in the countreset  $i = 127$  and  $j = 127$  , this means the computation is complete and we move to the reset state. We stay in the countreset state for 2 clock cycles to let the RAM write by maintaining a wait count. If wait count is 0 we move to countreset state elsif waitcount is 1 we transition to Read State again for the next set of products. We set cntrl equal to 0 , to set the accumulated sum to 0.
- From, the reset state, we always stay in it. We now take the input from the board to display the entries of the output matrix by reading from the RAM.

- We make a state transition each clock cycle, except in the countreset state, in which we wait for 2 clock cycles.

```

process(curstate)
begin
case curstate is
when reset =>
    wram<='0'; -- write disabled
    comp_en<='0'; --compute disabled
    nextstate<=reset;
    write_address_int<=(to_integer(unsigned(add)));
    dig3(3)<=ram_out(15);
    dig3(2)<=ram_out(14);
    dig3(1)<=ram_out(13);
    dig3(0)<=ram_out(12);
    dig2(3)<=ram_out(11);
    dig2(3)<=ram_out(10);
    dig2(3)<=ram_out(9);
    dig2(3)<=ram_out(8);
    dig1(3)<=ram_out(7);
    dig1(3)<=ram_out(6);
    dig1(3)<=ram_out(5);
    dig1(3)<=ram_out(4);
    dig0(3)<=ram_out(3);
    dig0(3)<=ram_out(2);
    dig0(3)<=ram_out(1);
    dig0(3)<=ram_out(0);

when read=>
    wreg<='1'; -- write register enabled . Now registers have been written, read from rom
    nextstate<=compute;

when write=>
    comp_en<='0'; -- computation disabled
    wram<='1'; -- write ram enabled
    nextstate<=countreset;

when compute =>
    wreg<='0'; -- register content wont be modified while computing
    k<=k+1;
    comp_en<='1';
    if (k<128) then
        nextstate<=read;
    elsif k = 128 then
        nextstate<= write;
    end if;

when countreset=>
    k<=0;
    if write_address_int =16383 then
        nextstate<=reset;
    else
        write_address_int<=write_address_int+1;
        nextstate<=read;
        if wait_count = 0 then
            nextstate<=countreset;
            wait_count<=1;
        elsif wait_count =1 then
            nextstate<=read;

```


```
--      wait_count<=0;
--      wram<='0';
--      write_address_int<=write_address_int+1;
--      end if;
--      end if;
--      cntrl<='1';
--      end case;

end process;

end machine;
```

Write address = 128 jtu

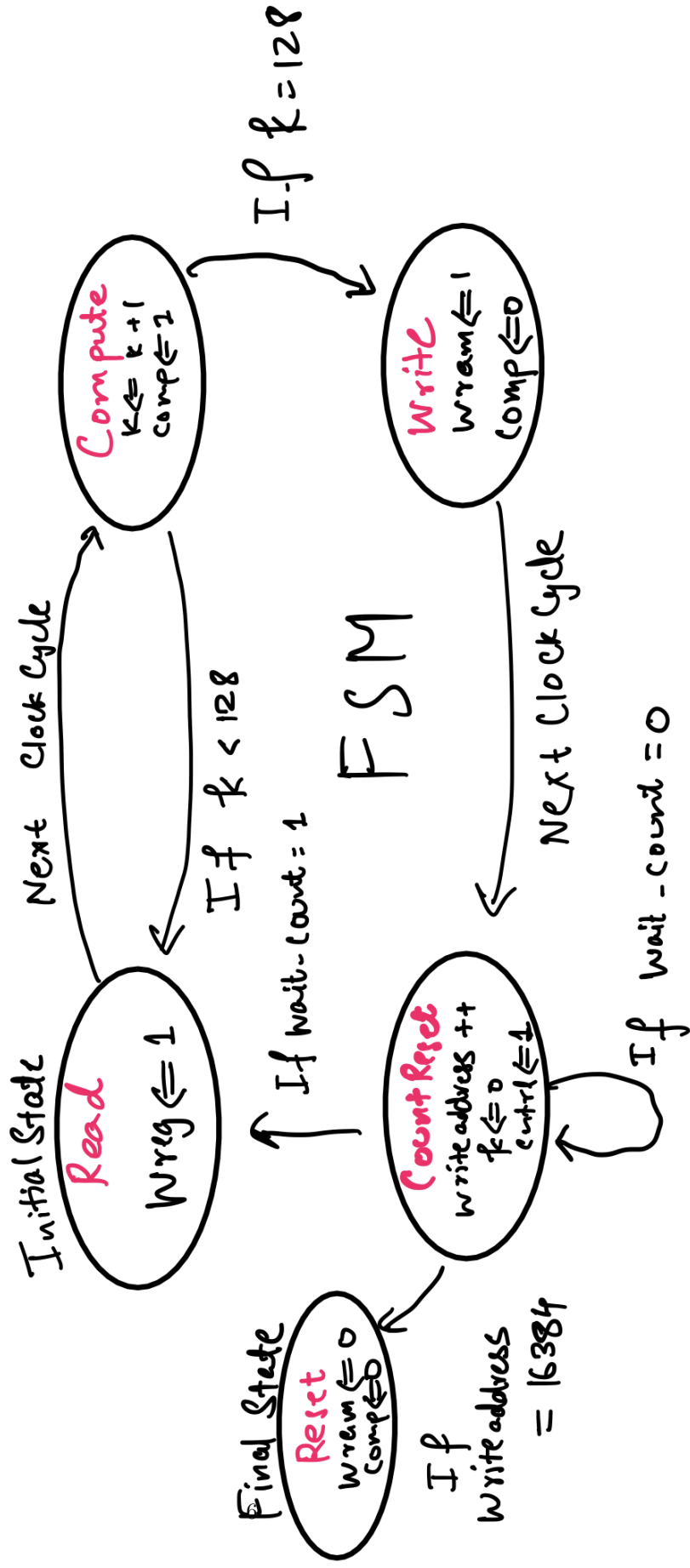$i = \text{write address} \% 128$      $j = \text{write address} // 128$



## 6 Block Diagram

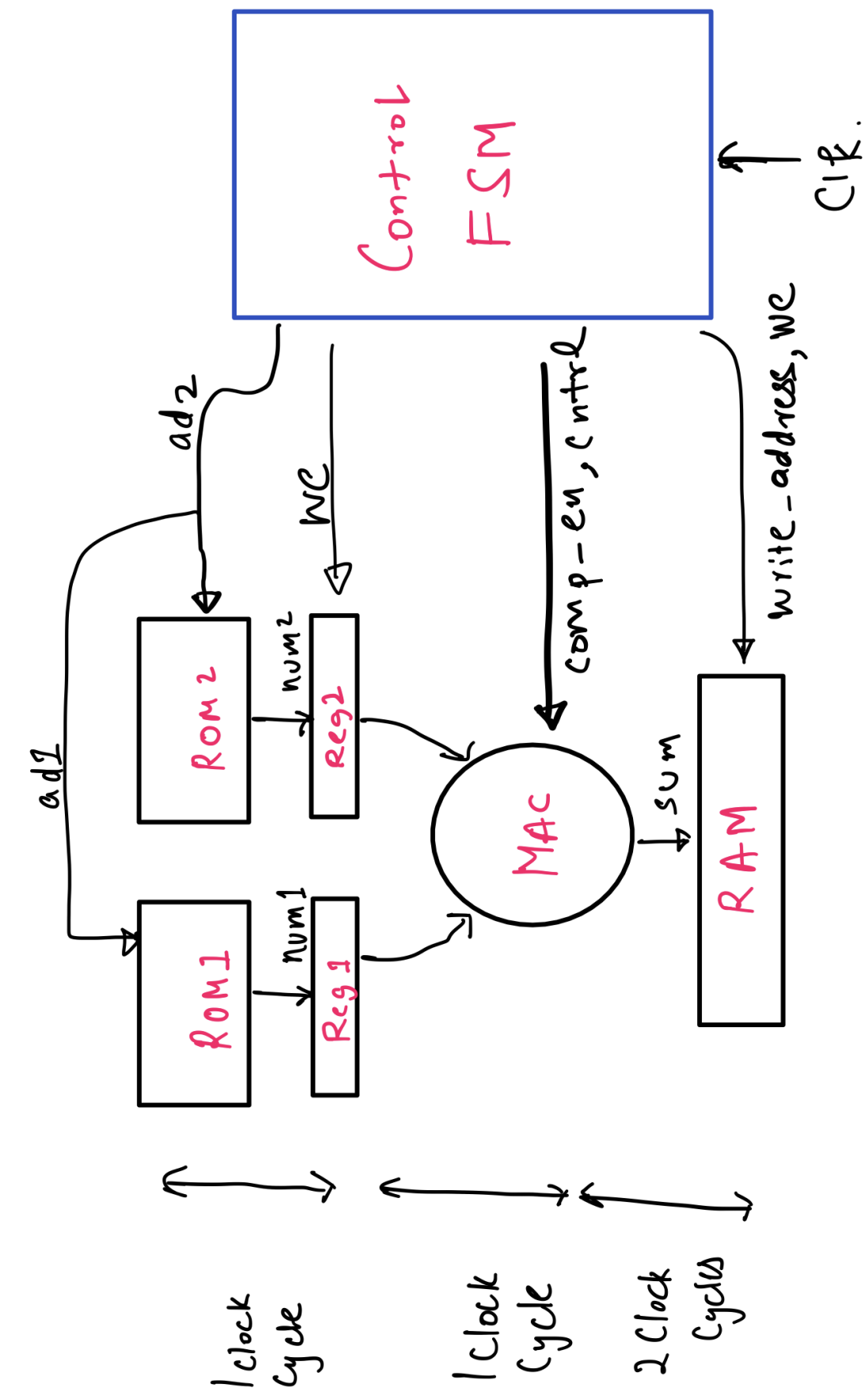


Figure 5:



## 7 Simulation Snapshots

 


Figure 6: We can see that after  $k = 128$  we go to countreset state, sum is reset to 0





Resource	Utilization	Available	Utilization %
LUT	6813	20800	32.75
LUTRAM	1792	9600	18.67
FF	500	41600	1.20
IO	26	106	24.53

 


Figure 9: Resource Utilization

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

**Total On-Chip Power:** 0.106 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 25.5°C  
 Thermal Margin: 59.5°C (11.8 W)  
 Effective  $\theta_{JA}$ : 5.0°C/W  
 Power supplied to off-chip devices: 0 W  
 Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

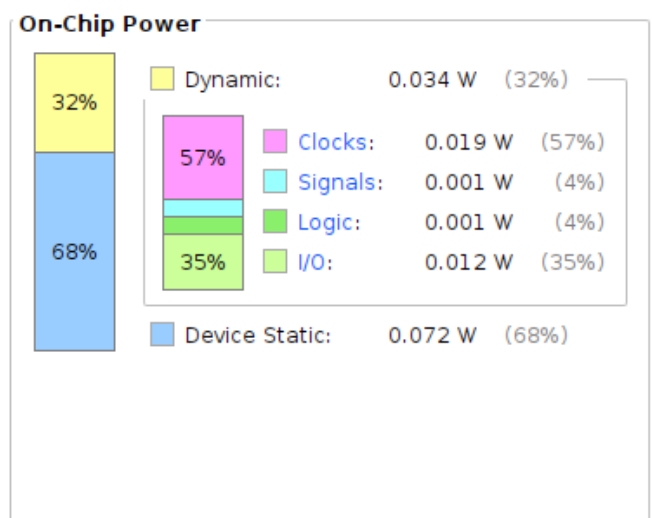


Figure 10: Power Utilization

## 8 Test Cases

We show the output on the board for some indices.

 


Figure 11: 0th index for  $M^2$ , where M is the sample matrix given

 


Figure 12:

 


Figure 13: